Self-Project

Topic: Implementation of 8x8 bit Dadda Multiplier

Name: Vipin Kumar Roll No: 213070102

Mtech 2nd year - EE7(SSD)

Dadda Multipliers:


- 1. Generate all bits of the partial products in parallel.
- 2. Collect all partial products bits with the same place value in bunches of wires and reduce these in several layers of adders till each weight has no more than two wires.
- 3. For all bit positions which have two wires, take one wire at corresponding place values to form one number, and the other wire to form another number.

Add these two numbers using a fast adder of appropriate size.


- Dadda multipliers are very similar to Wallace multipliers
 - Wallace multipliers reduce as soon as possible, while Dadda multipliers reduce as late as possible.
 - ➤ Dadda multipliers plan on reducing the final number of wires for any weight to 2 with as few and as small adders as possible.
 - ➤ We determine the number of layers required first, beginning from the last layer, where no more than 2 wires should be left.
 - ➤ The number of layers in Dadda multipliers is the same as in Wallace multipliers.
- We work back from the final adder to earlier layers till we find that we can manage all wires generated by the partial product generator.
- We know that the final adder can take no more than 2 wires for each weight
- Let dj represent the maximum number of wires for any weight in layer j, where j = 1 for the final adder. (Thus d1 = 2).
- The maximum number of wires which can be handled in layer j+1 (from the end) is the integral part of 3/2dj.

• We go up in j, till we reach a number which is just greater than or equal to the largest bunch of wires in any weight. The number of reduction layers required is this final j -1.

Simulated Result in Binary:

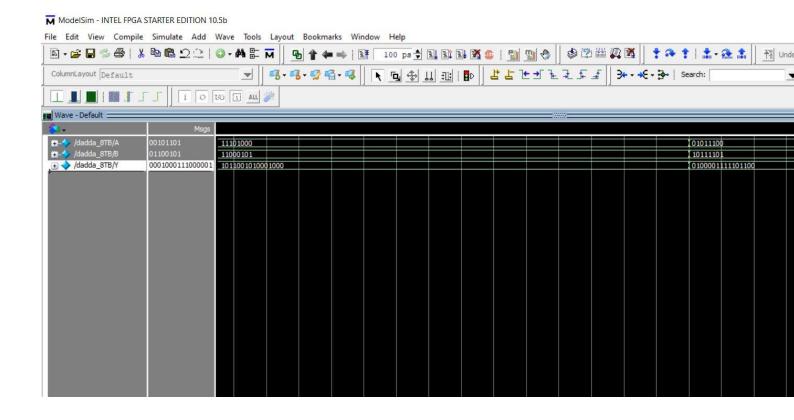

Simulated result in Unsigned format:

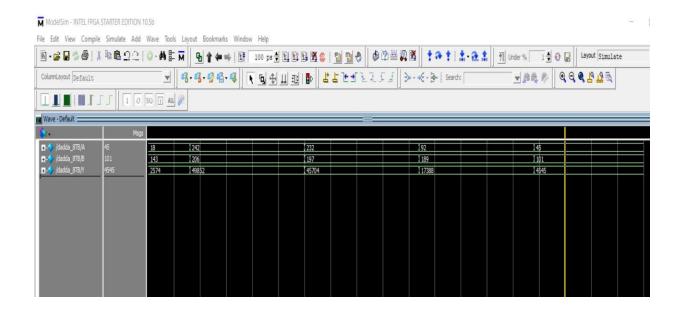

```
# run -all
 A= 36, B=129, AxB= 4644
# A= 9,B= 99,AxB= 891
# A= 13, B=141, AxB= 1833
# A=101, B= 18, AxB= 1818
      1,B= 13,AxB= 13
# A=118,B= 61,AxB= 7198
# A=237, B=140, AxB=33180
# A=249, B=198, AxB=49302
# A=197, B=170, AxB=33490
# A=229, B=119, AxB=27251
# A= 18, B=143, AxB= 2574
# A=242, B=206, AxB=49852
# A=232, B=197, AxB=45704
# A= 92, B=189, AxB=17388
# A= 45, B=101, AxB= 4545
```

Verilog code:

```
// Designing in Half Adder
// Sum = a XOR b, Cout = a AND b
```

module HA(a, b, Sum, Cout);

```
input a, b; // a and b are inputs with size 1-bit
output Sum, Cout; // Sum and Cout are outputs with size 1-bit
assign Sum = a ^ b;
assign Cout = a & b;
endmodule
//carry save adder -- for implementing dadda multiplier
//csa for use of half adder and full adder.
module csa_dadda(A,B,Cin,Y,Cout);
input A,B,Cin;
output Y,Cout;
assign Y = A^B^Cin;
assign Cout = (A\&B)|(A\&Cin)|(B\&Cin);
endmodule
// dadda multiplier
```

```
// A - 8 bits , B - 8bits, y(output) - 16bits
module dadda(A,B,y);
  input [7:0] A;
  input [7:0] B;
  output wire [15:0] y;
  wire gen_pp [0:7][7:0];
// stage-1 sum and carry
  wire [0:5]s1,c1;
// stage-2 sum and carry
  wire [0:13]s2,c2;
// stage-3 sum and carry
  wire [0:9]s3,c3;
// stage-4 sum and carry
  wire [0:11]s4,c4;
// stage-5 sum and carry
  wire [0:13]s5,c5;
```

// generating partial products

```
//// j=0

assign gen_pp[0][0] = A[0]*B[0];

assign gen_pp[1][0] = A[0]*B[1];

assign gen_pp[2][0] = A[0]*B[2];

assign gen_pp[3][0] = A[0]*B[3];

assign gen_pp[4][0] = A[0]*B[4];

assign gen_pp[5][0] = A[0]*B[5];

assign gen_pp[6][0] = A[0]*B[6];

assign gen_pp[7][0] = A[0]*B[7];
```

//// j=1 assign gen_pp[0][1] = A[1]*B[0]; assign gen_pp[1][1] = A[1]*B[1]; assign gen_pp[2][1] = A[1]*B[2]; assign gen_pp[3][1] = A[1]*B[3]; assign gen_pp[4][1] = A[1]*B[4]; assign gen_pp[5][1] = A[1]*B[5]; assign gen_pp[6][1] = A[1]*B[6]; assign gen_pp[7][1] = A[1]*B[7];

```
//// j=2
assign gen_pp[0][2] = A[2]*B[0];
assign gen_pp[1][2] = A[2]*B[1];
assign gen_pp[2][2] = A[2]*B[2];
assign gen_pp[3][2] = A[2]*B[3];
assign gen pp[4][2] = A[2]*B[4];
assign gen pp[5][2] = A[2]*B[5];
assign gen_pp[6][2] = A[2]*B[6];
assign gen pp[7][2] = A[2]*B[7];
//// j=3
assign gen_pp[0][3] = A[3]*B[0];
assign gen_pp[1][3] = A[3]*B[1];
assign gen_pp[2][3] = A[3]*B[2];
assign gen pp[3][3] = A[3]*B[3];
assign gen_pp[4][3] = A[3]*B[4];
assign gen_pp[5][3] = A[3]*B[5];
assign gen_pp[6][3] = A[3]*B[6];
assign gen pp[7][3] = A[3]*B[7];
//// j=4
assign gen_pp[0][4] = A[4]*B[0];
assign gen_pp[1][4] = A[4]*B[1];
```

```
assign gen_pp[2][4] = A[4]*B[2];
assign gen_pp[3][4] = A[4]*B[3];
assign gen_pp[4][4] = A[4]*B[4];
assign gen_pp[5][4] = A[4]*B[5];
assign gen_pp[6][4] = A[4]*B[6];
assign gen pp[7][4] = A[4]*B[7];
//// j=5
assign gen pp[0][5] = A[5]*B[0];
assign gen_pp[1][5] = A[5]*B[1];
assign gen_pp[2][5] = A[5]*B[2];
assign gen pp[3][5] = A[5]*B[3];
assign gen_pp[4][5] = A[5]*B[4];
assign gen pp[5][5] = A[5]*B[5];
assign gen pp[6][5] = A[5]*B[6];
assign gen_pp[7][5] = A[5]*B[7];
//// j=6
assign gen_pp[0][6] = A[6]*B[0];
assign gen_pp[1][6] = A[6]*B[1];
assign gen_pp[2][6] = A[6]*B[2];
assign gen_pp[3][6] = A[6]*B[3];
```

```
assign gen pp[4][6] = A[6]*B[4];
assign gen_pp[5][6] = A[6]*B[5];
assign gen pp[6][6] = A[6]*B[6];
assign gen pp[7][6] = A[6]*B[7];
//// j=7
assign gen_pp[0][7] = A[7]*B[0];
assign gen pp[1][7] = A[7]*B[1];
assign gen pp[2][7] = A[7]*B[2];
assign gen pp[3][7] = A[7]*B[3];
assign gen pp[4][7] = A[7]*B[4];
assign gen pp[5][7] = A[7]*B[5];
assign gen pp[6][7] = A[7]*B[6];
assign gen pp[7][7] = A[7]*B[7];
```

```
//Reduction by stages.
// di_values = 2,3,4,6,8,13...
```

```
HA h1(.a(gen_pp[6][0]),.b(gen_pp[5][1]),.Sum(s1[0]),.Cout(c1[0]));
  HA h2(.a(gen pp[4][3]),.b(gen pp[3][4]),.Sum(s1[2]),.Cout(c1[2]));
  HA h3(.a(gen pp[4][4]),.b(gen pp[3][5]),.Sum(s1[4]),.Cout(c1[4]));
  csa dadda
c11(.A(gen pp[7][0]),.B(gen pp[6][1]),.Cin(gen pp[5][2]),.Y(s1[1]),.C
out(c1[1]));
  csa_dadda
c12(.A(gen_pp[7][1]),.B(gen_pp[6][2]),.Cin(gen_pp[5][3]),.Y(s1[3]),.C
out(c1[3]));
  csa dadda
c13(.A(gen pp[7][2]),.B(gen pp[6][3]),.Cin(gen pp[5][4]),.Y(s1[5]),.C
out(c1[5]));
//Stage 2 - reducing fom 6 to 4
  HA h4(.a(gen pp[4][0]),.b(gen pp[3][1]),.Sum(s2[0]),.Cout(c2[0]));
  HA h5(.a(gen_pp[2][3]),.b(gen_pp[1][4]),.Sum(s2[2]),.Cout(c2[2]));
```

```
csa dadda
c21(.A(gen pp[5][0]),.B(gen pp[4][1]),.Cin(gen pp[3][2]),.Y(s2[1]),.C
out(c2[1]));
  csa dadda
c22(.A(s1[0]),.B(gen_pp[4][2]),.Cin(gen_pp[3][3]),.Y(s2[3]),.Cout(c2[3]
));
  csa dadda
c23(.A(gen pp[2][4]),.B(gen pp[1][5]),.Cin(gen pp[0][6]),.Y(s2[4]),.C
out(c2[4]));
  csa dadda c24(.A(s1[1]),.B(s1[2]),.Cin(c1[0]),.Y(s2[5]),.Cout(c2[5]));
  csa dadda
c25(.A(gen pp[2][5]),.B(gen pp[1][6]),.Cin(gen pp[0][7]),.Y(s2[6]),.C
out(c2[6]));
  csa dadda c26(.A(s1[3]),.B(s1[4]),.Cin(c1[1]),.Y(s2[7]),.Cout(c2[7]));
  csa_dadda
c27(.A(c1[2]),.B(gen pp[2][6]),.Cin(gen pp[1][7]),.Y(s2[8]),.Cout(c2[8
]));
  csa dadda c28(.A(s1[5]),.B(c1[3]),.Cin(c1[4]),.Y(s2[9]),.Cout(c2[9]));
  csa dadda
c29(.A(gen pp[4][5]),.B(gen pp[3][6]),.Cin(gen pp[2][7]),.Y(s2[10]),.
Cout(c2[10]));
  csa dadda
c210(.A(gen pp[7][3]),.B(c1[5]),.Cin(gen pp[6][4]),.Y(s2[11]),.Cout(c2
[11]));
  csa dadda
c211(.A(gen_pp[5][5]),.B(gen_pp[4][6]),.Cin(gen_pp[3][7]),.Y(s2[12]),.
Cout(c2[12]));
```

```
csa dadda
c212(.A(gen_pp[7][4]),.B(gen_pp[6][5]),.Cin(gen_pp[5][6]),.Y(s2[13]),.
Cout(c2[13]));
//Stage 3 - reducing fom 4 to 3
  HA h6(.a(gen_pp[3][0]),.b(gen_pp[2][1]),.Sum(s3[0]),.Cout(c3[0]));
  csa dadda
c31(.A(s2[0]),.B(gen_pp[2][2]),.Cin(gen_pp[1][3]),.Y(s3[1]),.Cout(c3[1]
));
  csa_dadda c32(.A(s2[1]),.B(s2[2]),.Cin(c2[0]),.Y(s3[2]),.Cout(c3[2]));
  csa dadda c33(.A(c2[1]),.B(c2[2]),.Cin(s2[3]),.Y(s3[3]),.Cout(c3[3]));
  csa dadda c34(.A(c2[3]),.B(c2[4]),.Cin(s2[5]),.Y(s3[4]),.Cout(c3[4]));
  csa dadda c35(.A(c2[5]),.B(c2[6]),.Cin(s2[7]),.Y(s3[5]),.Cout(c3[5]));
  csa dadda c36(.A(c2[7]),.B(c2[8]),.Cin(s2[9]),.Y(s3[6]),.Cout(c3[6]));
  csa dadda
c37(.A(c2[9]),.B(c2[10]),.Cin(s2[11]),.Y(s3[7]),.Cout(c3[7]));
  csa dadda
c38(.A(c2[11]),.B(c2[12]),.Cin(s2[13]),.Y(s3[8]),.Cout(c3[8]));
  csa dadda
c39(.A(gen_pp[7][5]),.B(gen_pp[6][6]),.Cin(gen_pp[5][7]),.Y(s3[9]),.C
out(c3[9]));
//Stage 4 - reducing fom 3 to 2
```

```
HA h7(.a(gen pp[2][0]),.b(gen pp[1][1]),.Sum(s4[0]),.Cout(c4[0]));
```

```
csa\_dadda
c41(.A(s3[0]),.B(gen pp[1][2]),.Cin(gen pp[0][3]),.Y(s4[1]),.Cout(c4[1]
));
  csa dadda
c42(.A(c3[0]),.B(s3[1]),.Cin(gen_pp[0][4]),.Y(s4[2]),.Cout(c4[2]));
  csa dadda
c43(.A(c3[1]),.B(s3[2]),.Cin(gen_pp[0][5]),.Y(s4[3]),.Cout(c4[3]));
  csa dadda c44(.A(c3[2]),.B(s3[3]),.Cin(s2[4]),.Y(s4[4]),.Cout(c4[4]));
  csa dadda c45(.A(c3[3]),.B(s3[4]),.Cin(s2[6]),.Y(s4[5]),.Cout(c4[5]));
  csa dadda c46(.A(c3[4]),.B(s3[5]),.Cin(s2[8]),.Y(s4[6]),.Cout(c4[6]));
  csa dadda
c47(.A(c3[5]),.B(s3[6]),.Cin(s2[10]),.Y(s4[7]),.Cout(c4[7]));
  csa dadda
c48(.A(c3[6]),.B(s3[7]),.Cin(s2[12]),.Y(s4[8]),.Cout(c4[8]));
  csa dadda
c49(.A(c3[7]),.B(s3[8]),.Cin(gen pp[4][7]),.Y(s4[9]),.Cout(c4[9]));
  csa dadda
c410(.A(c3[8]),.B(s3[9]),.Cin(c2[13]),.Y(s4[10]),.Cout(c4[10]));
  csa dadda
c411(.A(c3[9]),.B(gen_pp[7][6]),.Cin(gen_pp[6][7]),.Y(s4[11]),.Cout(c4
[11]));
//Stage 5 - reducing fom 2 to 1
  // adding total sum and carry to get final output
```

```
csa dadda
c51(.A(s4[0]),.B(gen pp[0][2]),.Cin(c5[0]),.Y(y[2]),.Cout(c5[1]));
  csa dadda c52(.A(c4[0]),.B(s4[1]),.Cin(c5[1]),.Y(y[3]),.Cout(c5[2]));
  csa dadda c54(.A(c4[1]),.B(s4[2]),.Cin(c5[2]),.Y(y[4]),.Cout(c5[3]));
  csa dadda c55(.A(c4[2]),.B(s4[3]),.Cin(c5[3]),.Y(y[5]),.Cout(c5[4]));
  csa dadda c56(.A(c4[3]),.B(s4[4]),.Cin(c5[4]),.Y(y[6]),.Cout(c5[5]));
  csa dadda c57(.A(c4[4]),.B(s4[5]),.Cin(c5[5]),.Y(y[7]),.Cout(c5[6]));
  csa dadda c58(.A(c4[5]),.B(s4[6]),.Cin(c5[6]),.Y(y[8]),.Cout(c5[7]));
  csa dadda c59(.A(c4[6]),.B(s4[7]),.Cin(c5[7]),.Y(y[9]),.Cout(c5[8]));
  csa dadda
c510(.A(c4[7]),.B(s4[8]),.Cin(c5[8]),.Y(y[10]),.Cout(c5[9]));
  csa dadda
c511(.A(c4[8]),.B(s4[9]),.Cin(c5[9]),.Y(y[11]),.Cout(c5[10]));
  csa dadda
c512(.A(c4[9]),.B(s4[10]),.Cin(c5[10]),.Y(y[12]),.Cout(c5[11]));
  csa dadda
c513(.A(c4[10]),.B(s4[11]),.Cin(c5[11]),.Y(y[13]),.Cout(c5[12]));
  csa dadda
c514(.A(c4[11]),.B(gen pp[7][7]),.Cin(c5[12]),.Y(y[14]),.Cout(c5[13]));
```

```
assign y[0] = gen_pp[0][0];
assign y[15] = c5[13];
```

endmodule